

HalfAdder_qiskit

December 21, 2020

1 Half Adder Quantum Circuit (v1.0)

The following is a quantum implementation of the classical Half Adder circuit. The image below is the classical implementation of a Half Adder with a XOR and AND gate for Sum and Carry respectively.

```
[7]: from qiskit import *  
from qiskit.tools.visualization import plot_bloch_multivector  
from qiskit.tools.visualization import plot_histogram
```

1.0.1 Defining the Circuit

```
[14]: quantReg = QuantumRegister(4)  
classReg = ClassicalRegister(2)  
circuit = QuantumCircuit(quantReg, classReg)
```


```
[15]: circuit.x(0) #Comment out this line to make A = 0  
circuit.x(1) #Comment out this line to make B = 0  
circuit.barrier()
```

```
[15]: <qiskit.circuit.instructionset.InstructionSet at 0x1c22a935580>
```

The above line allows the user to test out the different variations for the Half Adder. By default it is set to A = 1 and B = 1. If the user wants to change the gates they will have to run the simulator and the output again.

```
[16]: %matplotlib inline  
circuit.draw(output = 'mpl')
```

```
[16]:
```

 


1.0.2 Performing the Sum Operation

In the classical working of the Half Adder, the Sum is calculated by XORing A and B. In a quantum circuit, the Controlled NOT (or CNOT for short) gate performs this operation

```
[17]: circuit.cx(0,2)
      circuit.cx(1,2)
      circuit.barrier()
      circuit.draw(output = 'mpl')
```

[17]:

 


A trivial point to note is that $q_0 \text{ CX } q_1 \sim q_0 \text{ XOR } q_1$. The value of the XOR is stored in q_1 . However, we don't want the value to be stored in q_1 , we want separate qubit to store it. So q_2 takes $q_1 \text{ XOR } (q_0 \text{ XOR } q_2)$. Since the default value of q_2 is 0 therefore $q_1 \text{ XOR } (q_0 \text{ XOR } q_2) = q_1 \text{ XOR } (q_0 \text{ XOR } 0) = (q_1 \text{ XOR } q_0) \text{ XOR } 0$. This does not affect the XOR result since if $(q_1 \text{ XOR } q_0) = 0$ then $(q_1 \text{ XOR } q_0) \text{ XOR } 0 = 0$ and the same applies for the 1 case.

1.0.3 Performing the Carry Operation

In the classical working of the Half Adder, the Carry is calculated by ANDing A and B. In a quantum circuit, the Toffoli CCNOT or CCX for short) gate performs this operation.


```
[19]: circuit.ccx(0,1,3)
      circuit.barrier()
      circuit.draw(output = 'mpl')
```

[19]:

 

```
[20]: circuit.measure(2,0)
      circuit.measure(3,1)
      circuit.draw(output = 'mpl')
```

[20]:

 


1.1 Results

```
[21]: nativeSim = Aer.get_backend('qasm_simulator')
      nativeResult = execute(circuit, backend = nativeSim).result()
      counts = nativeResult.get_counts()
```

1.1.1 Histogram Visualization

```
[22]: plot_histogram(counts)
```

[22]:

 


Since q_0 and q_1 are both 1 therefore $1 + 1 = 10$ ($S = 0$ and $C = 1$). We got the correct result. Yayy!

1.1.2 Bloch Sphere Visualization

```
[26]: nativeSVSim = Aer.get_backend('statevector_simulator')
      nativeSVResult = execute(circuit, backend = nativeSVSim).result()
      stateVector = nativeSVResult.get_statevector()
      plot_bloch_multivector(stateVector)
```

[26]:

 

Qubits 2 and 3 are the Sum and the Carry respectively. Once again, the correct result but just in a different visual format.